

Frequency Response of the CS Amplifier ($R_L = \infty$)