

Frequency Response of the CS Amplifier ( $R_L = \infty$ )

